



Department of Computing and Information System

Md. Selim Hossain, Senior Lecturer, CIS, DIU

1


Md. Selim Hossain, Senior Lecturer, CIS, DIU

Sequential And Combinational ALU

TYPES OF DIGITAL LOGIC CIRCUITS IN ALU

- COMBINATIONAL CIRCUITS
- SEQUENTIAL CIRCUITS

BLOCK DIAGRAM OF A COMBINATIONAL CIRCUIT

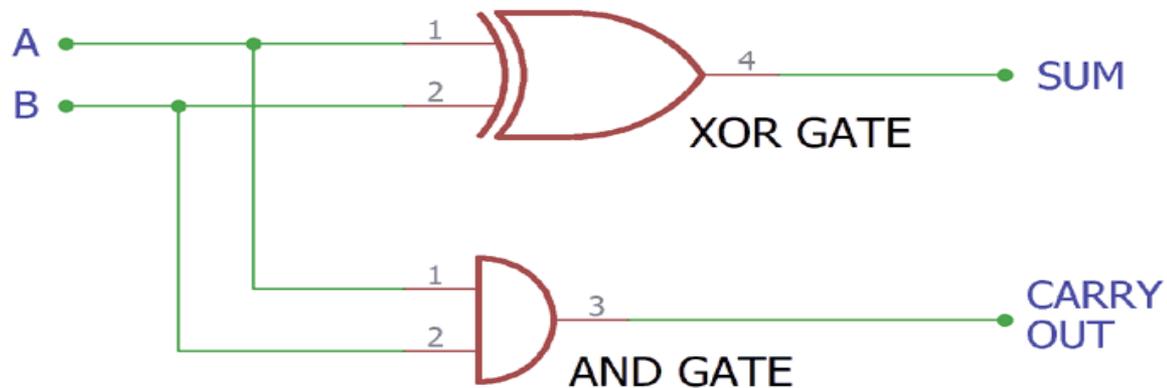

Half-Adder & Full-Adder

○ Half-Adder :

- A half-adder is a combinational circuit that performs the addition of two bits.

○ Full Adder :

- This type of adder is a little more difficult to implement than a half-adder.
- The main difference between a half-adder and a full-adder is that the full-adder has three inputs and two outputs.

x	y	z	S	C
0	0	0	0	0
0	0	1	1 ✓	0
0	1	0	1 ✓	0
0	1	1	0	1
1	0	0	1 ✓	0
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

$$\begin{aligned}
 S &= x'y'z + x'yz' + xy'z' + xyz \\
 &= x'(y'z + yz') + x(y'z' + yz) \\
 &= x'(y \oplus z) + x(y \oplus z)'
 \end{aligned}$$

$$= x'A + xA'$$

$$= x \oplus A$$

$$= x \oplus (y \oplus z)$$

$$A = y(+)z$$

$$\begin{aligned}
 C &= x'yz + xy'z + xyz' + xyz \\
 &= z(x'y + xy') + xy(z' + z) \\
 &= z(x(+)y) + xy \\
 &= z(x \oplus y) + xy
 \end{aligned}$$



Digital

Options

Step Size: 1

Units: Cycles Ticks


X Magnification: 8

Speed: 30


Breakpoint

Type: Level Edge

Condition: And Or

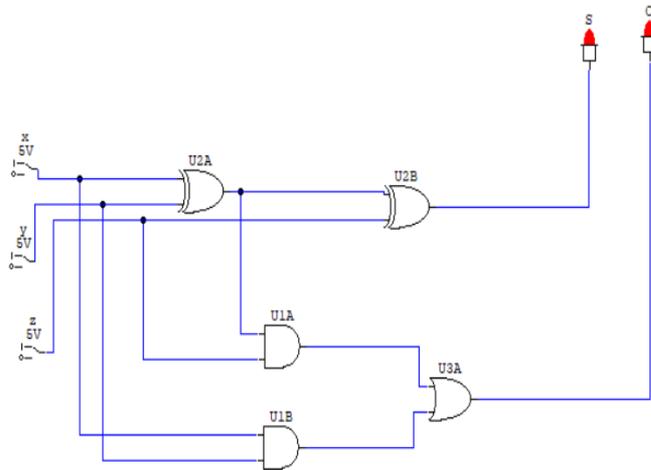

BLOCK DIAGRAM OF A SEQUENTIAL CIRCUIT

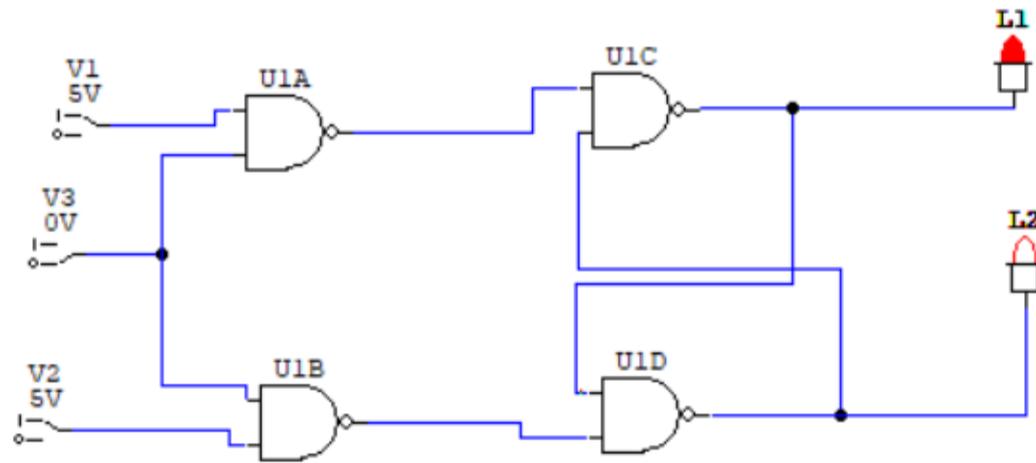

Thanks to All

Md. Selim Hossain, Senior Lecturer, CIS, DIU

9

Md. Selim Hossain, Senior Lecturer, CIS, DIU